

Understanding Trapped Antennas

By G8MNY


(Updated Feb 06)

(8 Bit ASCII Graphics use code page 473 or 850)

BASIC TRAP

Here is a simple 40m trap used in each side of an 80m dipole.

1/2 of the Dipole or a 1/4 wave wire

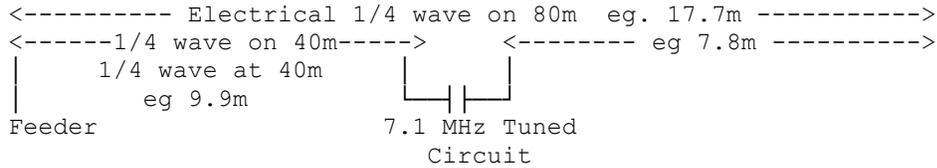

Note the 80m length is slightly shorter due to the added coil wire.

HOW IT WORKS

The L & C have to make a high impedance Z at 40m to isolate the hot end (high Z) of the 40m dipole.

$$Z = Q * Xc$$


This means the L must be quite large & C small to get the tuned circuit Q multiplied by the capacitance reactance Xc (= Xl at resonance) to make the Z very high.

The Voltage & Current rating is quite high, e.g. 2kV AC for 100W.

MULTIPLE BANDS

It is possible to add a series traps 1 per band, isolating the resonant aerial length from the rest.


1/2 of the Dipole or a 1/4 wave.

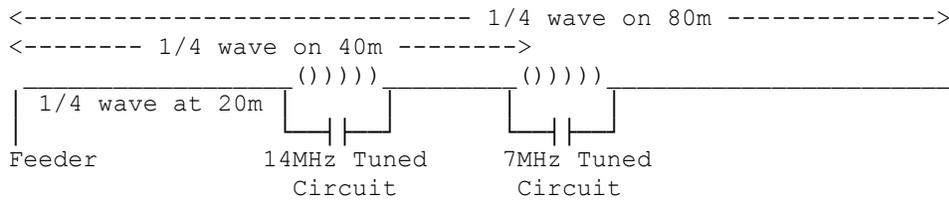

SOLID AERIALS

With solid aerials & beams the traps for say 10m & 15m are often combined. The outer sleeve forming both capacitors & also becoming the middle conductor, it is connected to a tapping on the coil.

1/2 Dipole or 1/4 wave vertical.

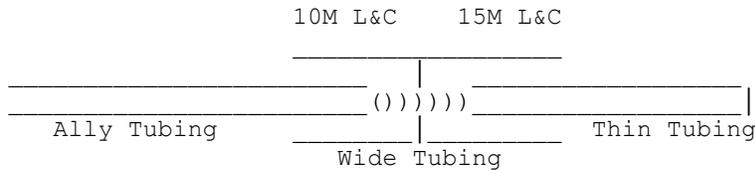

<-- 1/4 wave @ 10m -->

<----- 1/4 wave @ 15m ----->

<----- Electrical 1/4 wave @ 20m ----->

With this design water is a major problem, & drain holes are needed on the underside of the wide tubing.

Each length can sometimes be adjusted, so that the low SWR sweet spot can be set up per band, starting with the highest frequency.

POWER HANDLING

At resonance the trap voltage & current can be very high depending on the power. eg. @ 50W on half of a dipole @ say a Z of 10kΩ, means the trap has to isolate a voltage of :-

At 400W into say a vertical rod aerial the trap voltage could be:-

$$V = \sqrt{400 * 10,000} = 2 \text{ kV or } \pm 2.8 \text{ kV peak}$$

As the traps are not used (resonant) for the lowest band, generally they will not be power limited. e.g. a limit of 100W on 10m & 15m, but 400W on 20m is OK on a 10/15/20m tribander.

Why don't U send an interesting bul?

73 de John G8MNY @ GB7CIP