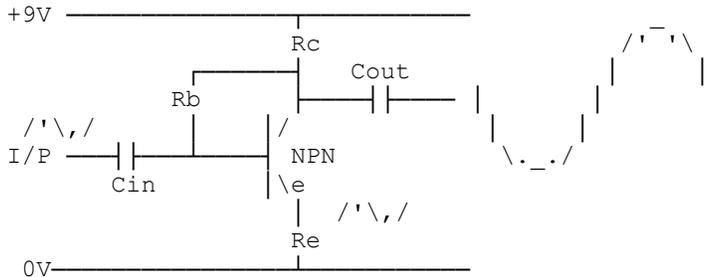


Subject: An AF amplifier stage

From: G8MNY@GB7CIP.#32.GBR.EU
 To : TECH@WW

By G8MNY (Updated Dec 04)
 This simple amplifier circuit is easy for calculations.



BASE BIAS $R = H_{fe} \times (R_c + R_e)$ Approx
 To get $\frac{1}{2}$ the DC swing on the O/P. This is because we want the same voltage C-E (almost the same as across R_b) as across the total load R of $R_c + R_e$.

GAIN = R_c / R_e approx (R_c may be lower due to external load).
 With high H_{fe} then I_e approx = I_c , so the emitter NFB R_e controls the collector current making the voltage gain just the voltage drop ratio of R_c / R_e . Assuming no external loads. For high gain applications R_e includes the internal emitter R of the transistor (typically a few ohms).

O/P $Z = X_{Cout} + (R_c // ((G-1) \times R_b))$
 This is the added components, including the apparent fraction of the bias R_b with load current in it.
 " //" means in parallel, many of the paralleled terms are insignificant. Technically the amount that $(G-1) \times R_b$ component that affects the O/P Z it will also depend the I/P source Z .


I/P $Z = X_{Cin} + ((H_{fe} \times R_e) // (R_b / (G+1)))$
 This is the added components, including the apparent fraction of the bias R_b with input current in it.
 " //" means in parallel, many of the paralleled terms are insignificant.

LF Roll off C_{in} & C_{out} affect the LF response. Basically each one will give -3dB & 6dB/Octave roll off when X_c equals the source + load Z_s .

HF Response
 Intrinsically limited by the transistor's FT when the H_{fe} becomes 1, & component layout (inter capacitance) causing Miller HF N.F.B. effects between O/P & I/P.

HF Compensation
 HF loss can be compensated for by putting a suitable C across R_e to give +3dB boost were $X_c = R_e$, eg. where the measure drop is -3dB. The 6dB/Octave lift after that should flatten the amp losses out. The input Z will be reduced at HF though. Not often used!

EXAMPLE

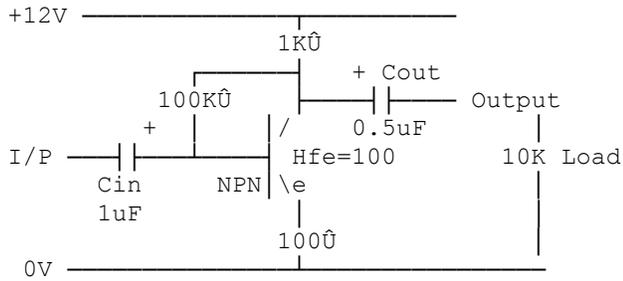

So in the above example Collector should be around +6V

Gain about 9 times

O/P Z about $900\Omega + X_{Cout}$

I/P Z about $5K\Omega + X_{Cin}$

LF response with Input source Z of zero, & O/P load of 10K...

I/P -3dB LF roll off, @ 31Hz where $X_c = 5K\Omega$ O/P -3dB LF roll off, @ 29Hz where $X_c = 10.9K\Omega$

Giving -6dB @ 30Hz & 12dB/Octave LF cut.

Why don't U send an interesting bul?

73 De John, G8MNY @ GB7CIP

/EX