

Locking a Frequency with 555


By G8MNY

(Updated Jan 16)

(8 Bit ASCII graphics use code page 437 or 850, Terminal Font)

Year ago I had a valve B&W 405 line camera that used many double triode astables to lock the 50Hz frame timebase to line interlaced 11250Hz line frequency! I reworked it for 625 line by raising the 2x line LC osc to 31250Hz & locking 4x 1/5 the frequency astables to it (>6250>1250>250>50Hz) to correctly lock the interlaced frame timebase.

The other day I had a similar problem, to lock an old 1980s stereo coder design to a modern RDS unit. This is normally done the other way around, locking RDS data unit from the 19kHz pilot! The trouble with my approach was there was no clean 57kHz to start with! The Pic RDS generator had 6 data bits added to synthesise the QPSK sine waves etc. So I used the MSB data to give the best 57kHz starting clock.

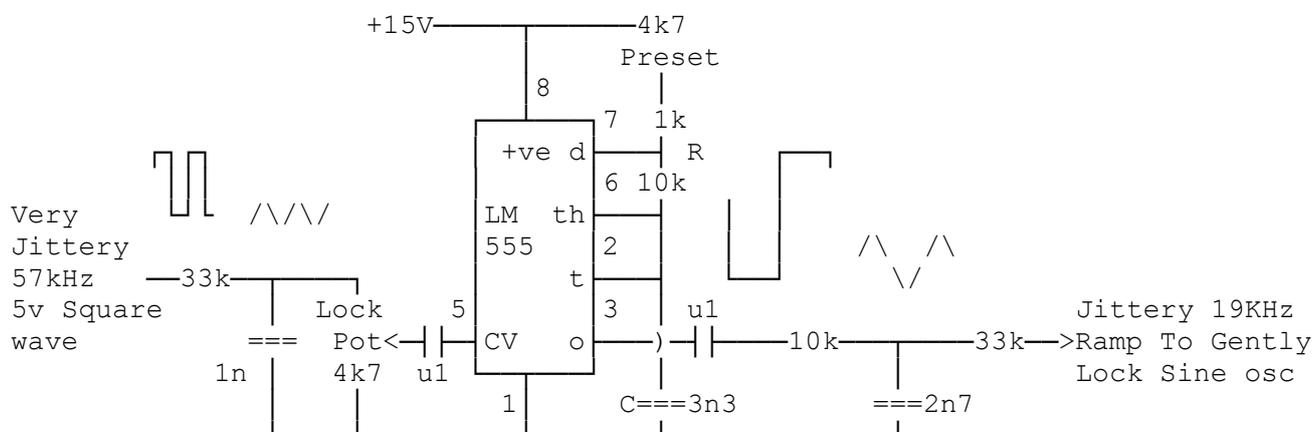

I found a slightly less jittery lock was obtained when both square waves were ramped to a triangle with a CR. The 555 19kHz astable is loosely locked to the 57kHz by modulating the Control Voltage rail used to compare the CR voltage. The smaller the lock input the more loosely locked (higher Q) result, but less stable to temp/Voltage changes. The C & R components that set the 19kHz need to be high stability types!

Result, after getting the ramps right & enough lock drive to the 555 astable @ 19kHz, it reliably locks up hot & cold, & with Wayne bridge sine osc gives a stable locked osc in the right phase too in my application!

The above principle can be used for up & down locking of different frequencies in many fractions etc. e.g. 50Hz from 60Hz.

See tech buls "Off Air Lock for Ref Osc.", & "Simple 1kHz AF Test Osc".

Why don't U send an interesting bul.

73 De John, G8MNY @ GB7CIP